GIRA

Manufacturers, products, systems

There's a Gira switch for almost everything in a Smart Home.

The solution you want – controlled by Gira.

We provide sophisticated, beautifully designed Smart Home solutions. Yet even if you decide to install building technology from other brands, you can still enjoy the high-quality design and functionality of our operating devices.

Many of our products work with systems and individual solutions from other manufacturers, which can then be controlled using our switches and other operating elements.

Gira One

KNX

Flush-mounted actuator

eNet

Various systems

EnOcean

24 volts

Bluetooth
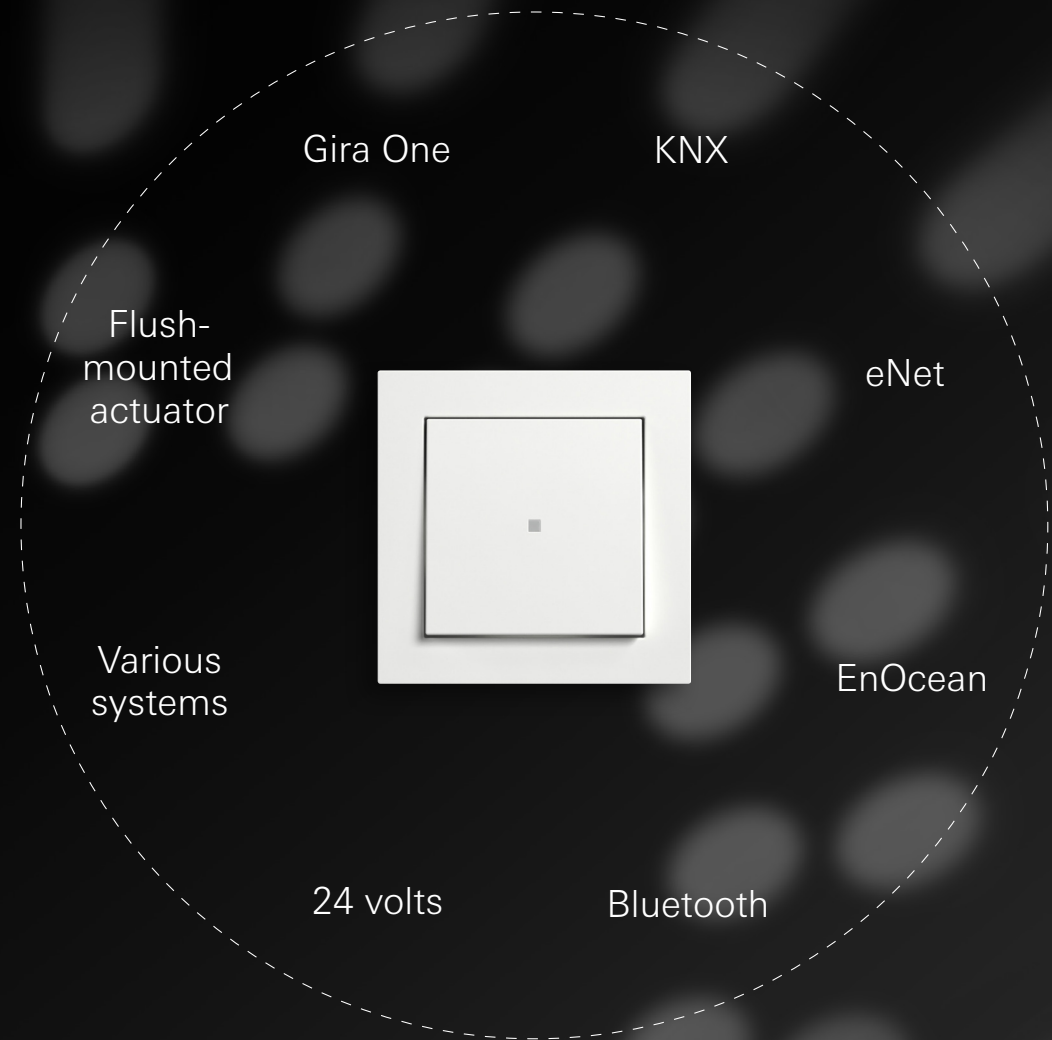
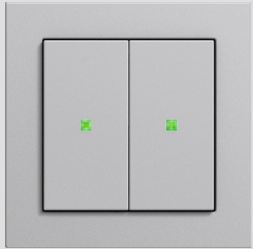# The KNX Smart Home: where other brands can also feel at home.

We offer comprehensive Smart Home solutions and systems based on KNX. What's more, Gira operating elements are compatible with solutions from a wide range of other providers via the KNX standard:
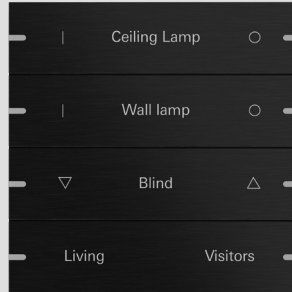
...and many more.

Operating devices
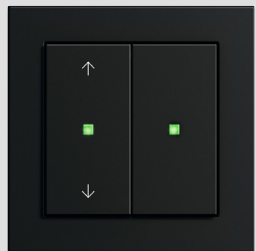

Buttons and pushbutton sensors (wired)

Button with rocker, 2-gang
for Gira One and KNX

Pushbutton sensor 4.55,
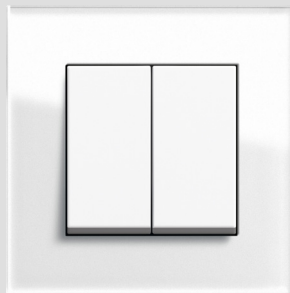3-gang for Gira One and KNX

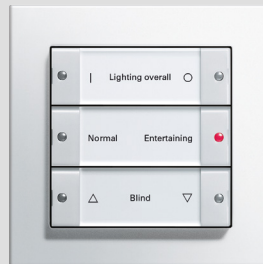Pushbutton sensor 4.95,
4-gang for Gira One and KNX

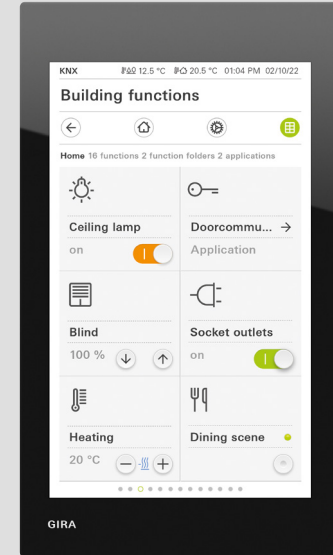**KNX RF operating devices
(wireless)**

RF operating top unit, 2-gang
Arrow symbols for KNX

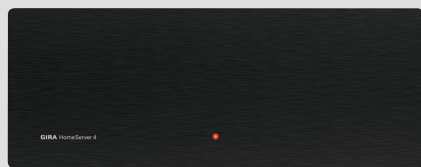RF wall transmitter, 2-gang
for KNX
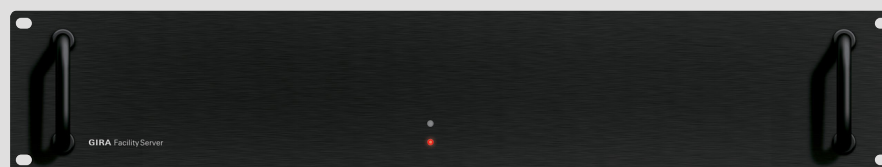
RF pushbutton sensor, 1-gang
for KNX

Gira G1
via network or WLAN

Other Gira products

Server
Gira HomeServer
Item no. 0529 00

Gira FacilityServer
Item no. 2075 00

Gira X1 server
Item no. 2096 00

Gira One server
Item no. 2039 00

Actuators
Switching actuator, 1-gang
16 A with 3-gang binary
input for Gira One and KNX
Item no. 5061 00

Dimming actuator, 1-gang
200 W with 3-gang binary
input for Gira One and KNX
Item no. 5065 00

Switching actuator,
4-gang 16 A with manual
actuation for KNX
Item no. 1004 00

Switching actuator,
4-gang 16 A with manual
actuation and current measurement
for C-load, for KNX
Item no. 1045 00

More information
is available at
partner.gira.com

Operating devices

# The eNet Smart Home offers brand diversity – with Gira at its core.

We have a whole range of operating elements, servers and actuators for the globally accepted eNet Smart Home standard. Thanks to the wireless protocol, you can easily integrate other products from manufacturers that are part of the eNet alliance. For example, smart radiator thermostats from tado or door communication from Siedle.

BRUMBERG   HÄFELE   JUNG
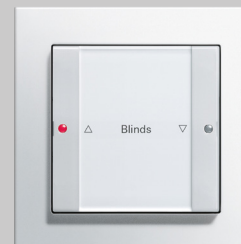
SSS SIEDLE   tado°
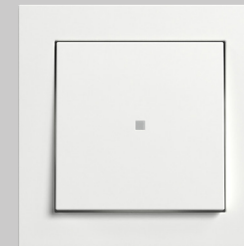
Buttons in the Gira System 3000

eNet wireless operating
top unit
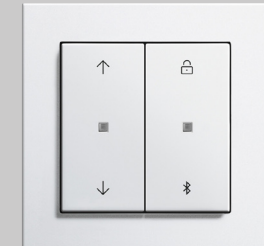
eNet wireless operating
top unit Memory

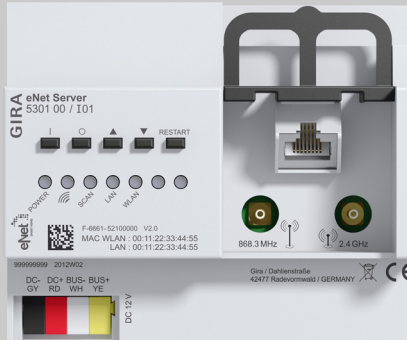eNet wireless wall
transmitter, 1-gang

eNet wireless hand-held
transmitter, 2-gang
Item no. 535210

eNet wireless hand-held
transmitter, 4-gang
Item no. 535410

Other Gira products

Server

eNet server
Item no. 530100

Actuators

eNet wireless switching/
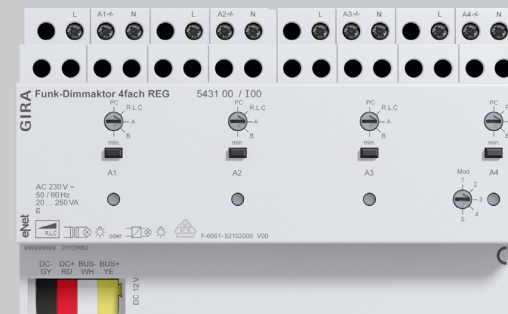momentary-contact actuator,
1-gang Mini
Item no. 5423 00

eNet wireless switching/
momentary-contact actuator,
1-gang Mini
Item no. 5420 50

eNet wireless
dimming actuator 1-gang,
Mini
Item no. 5420 00

eNet wireless dimming
actuator 1-gang DRA
Item no. 5423 00

eNet wireless dimming
actuator 4-gang DRA
Item no. 5431 00

eNet wireless
blind actuator, 1-gang
Item no. 5370 00

More information
is available at
partner.gira.com

As simple as WiFi: Gira transmits via the EnOcean system.

Loxone, Eltako, Viessmann, WAGO and others use the EnOcean wireless standard for their smart solutions. The standard is internationally recognised and can be used anywhere, similarly to WiFi or Bluetooth.

An EnOcean system can be operated seamlessly via Gira wireless wall transmitters.

Operating devices

Wireless wall transmitter
1-gang

Wireless wall transmitter
2-gang
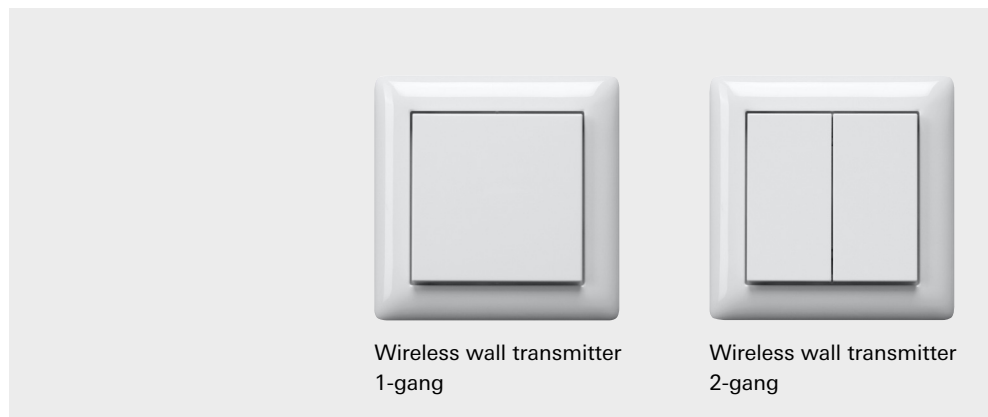
Green light for Bluetooth® applications.

Operating devices

Many brands and manufacturers, including Casambi, IKEA, Nanoleaf and Dyson, use the Bluetooth standard for lights and smart electrical devices. We also use a Bluetooth interface, for example in the BT wall transmitter or System 3000 top unit. This ensures that nothing hinders operation in the Gira design.

Learn more at
catalogue.gira.com
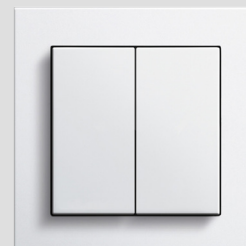
Bluetooth® wall transmitter,
2-gang

Gira System 3000
BT operating top unit

# We even work with 24 volts, in stage equipment for example.

Some Smart Home systems are based on 24-volt components, such as Loxone or DMX solutions (Digital Multiplex) in architecture and stage equipment. Gira operating devices can also be used for this purpose, as our pushbutton sensors and other wall buttons also work with 24 volts.

LOXONE **DMX** **ARDUINO**
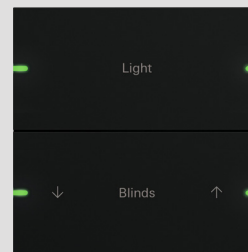
Operating devices

Pushbutton sensor 4.95,
24 V 2-gang
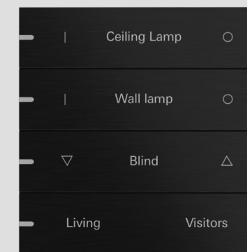
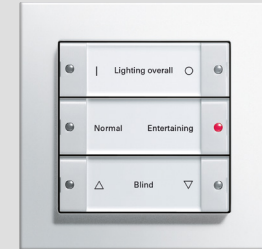Pushbutton sensor 4.95,
24 V 4-gang

Operating devices

No matter which Smart Home system is to be installed, if it is based on 24 V connections, many of our operating devices can be integrated into the systems. For example, the Gira pushbutton sensors 2 and 4 are equipped with zero-voltage contacts for maximum compatibility with solutions that use different operating voltages. These relays and actuators can usually be switched with Gira.
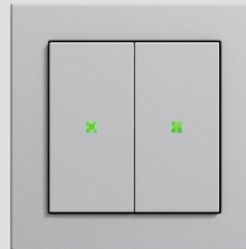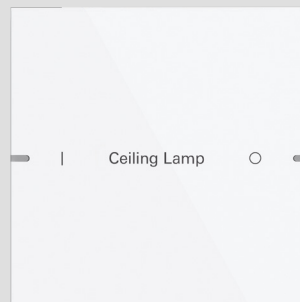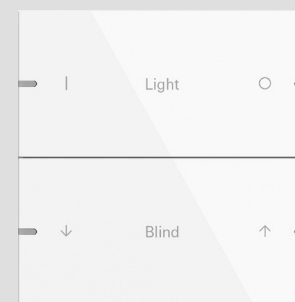
Rocker button, 4-gang

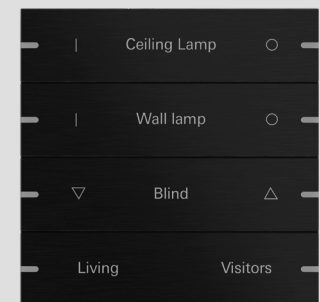Pushbutton sensor 2
1-gang 24 V zero-voltage

Pushbutton sensor 2, 3-gang
24 V zero-voltage

Pushbutton sensor 4.95,
24 V 1-gang

Pushbutton sensor 4.95,
24 V 2-gang

Pushbutton sensor 4.95,
24 V 4-gang

# Flush-mounted inserts and relays of all kinds speak "Gira".

Casambi, Nexentro, Frogblue, Shelly, Eltako and many more: some of our operating devices can be easily integrated into the respective wireless systems. This simply requires the appropriate transponder to be mounted on the flush-mounted insert and tucked away in the flush-mounted box.
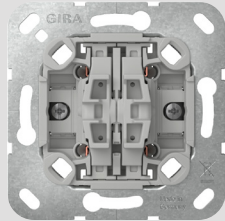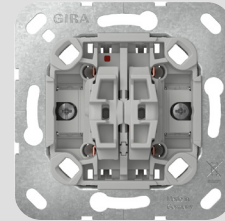
Operating devices
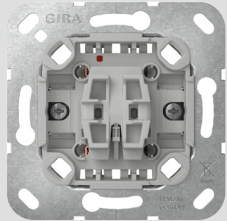
Rocker button
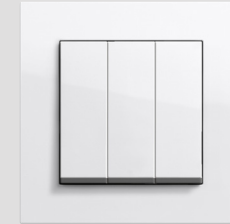(with claws)
Item no. 3151 00
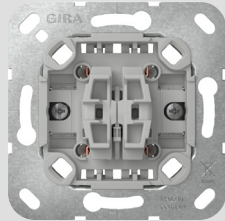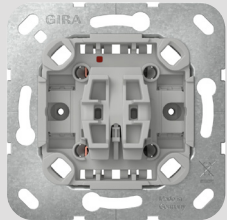
Rocker button, 2-gang
(with claws)
Item no. 3155 00

Rocker button, 4-gang
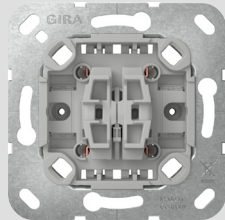(with claws)
Item no. 3147 00
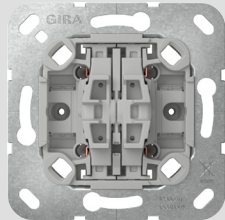
Blind rocker button
(with claws)
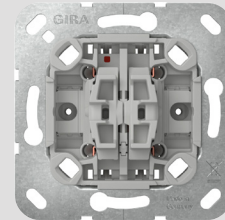Item no. 3158 00

Rocker button,
3-gang 10 A 250 V~

Rocker button
(without claws)
Item no. 3871 00

Rocker button, 2-gang
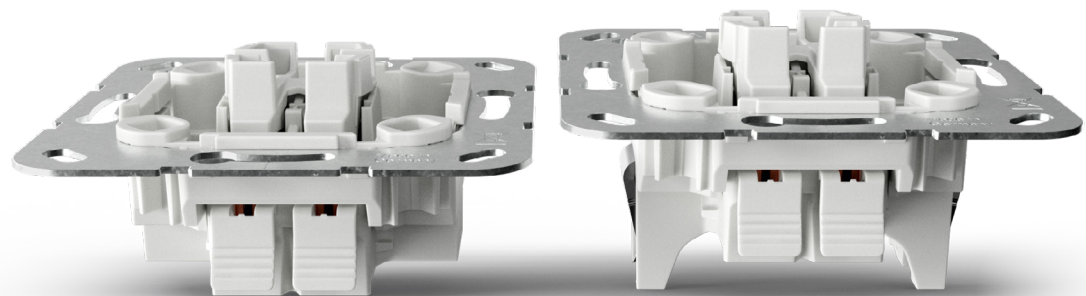(without claws)
Item no. 3875 00

Rocker button, 4-gang
(without claws)
Item no. 3867 00

Blind rocker button
(without claws)
Item no. 3878 00

Note:

We recommend the
variant without claws,
due to the reduced
installation depth and
the limited space in
the flush-mounted
box.

So, now you know a bit more – but do you still have questions?

We do not only communicate with KNX, Bluetooth, eNet, EnOcean and with many Smart Home brands:
we would also be happy to talk to you to discuss how you can connect Gira operating elements and other components to your Smart Home solution.

Feel free to contact us by sending your questions to info@gira.com

GIRA